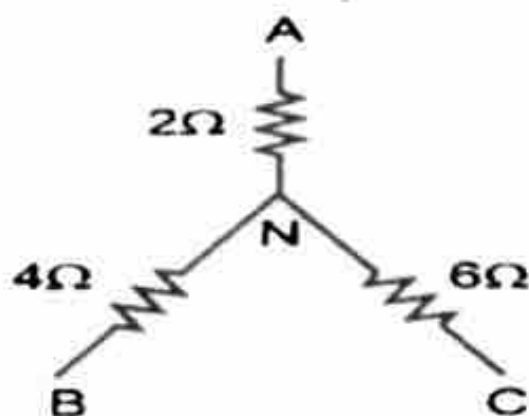


(a) Convert the star circuit into its equivalent delta circuit




(b) Write down the relation between line current and phase current, line voltage and phase voltage, power in balanced three phase delta connected balanced load.

(c) Explain the concept of back emf in a DC motor.

(d) What are the losses in a single-phase transformer?

(e) Draw and explain the construction diagram of LED and enlist the applications.

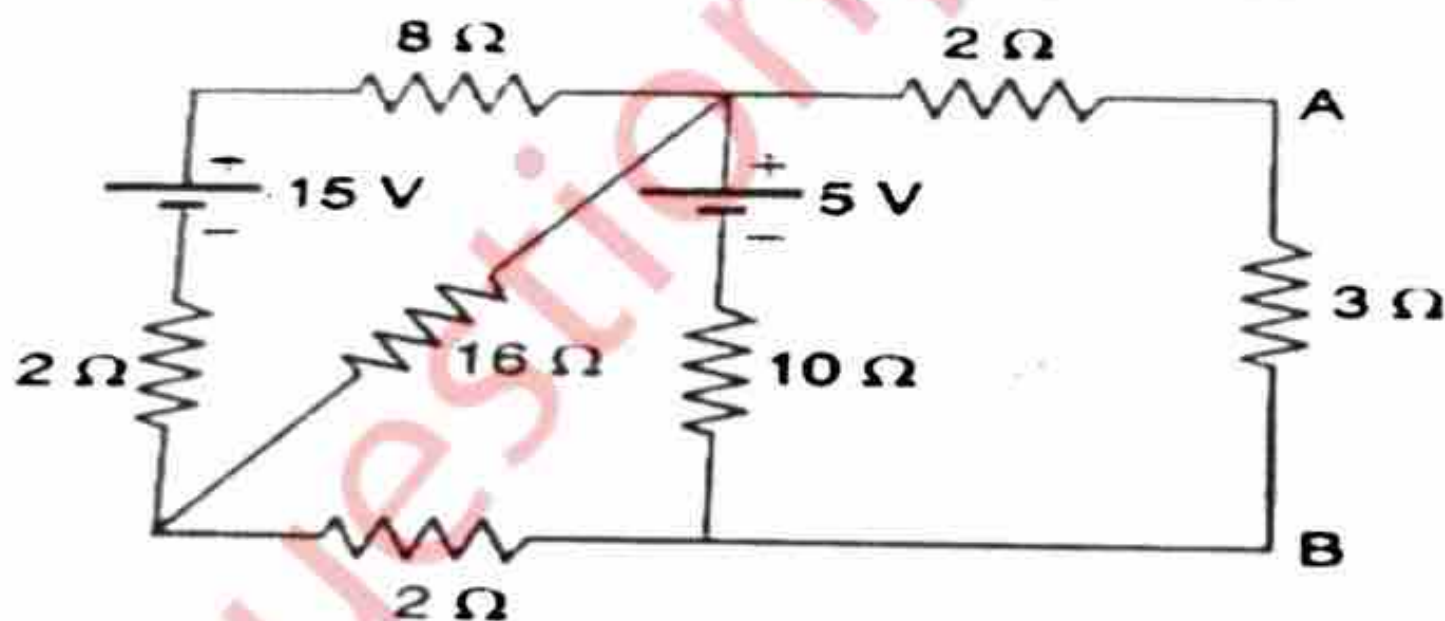(a) Using Norton's theorem, calculate the current through 3Ω resistor across the terminals A and B in the given circuit.



(b) Explain the working principle of three phase induction motor and mention its types.